

UNIT IV FAULT ANALYSIS - UNBALANCED FAULT

①

Introduction :-

The unsymmetrical faults are the faults in which the fault currents in the 3 phases are unequal. The different types of unsymmetrical faults are

- 1) Single line to cond fault
- 2) line to line fault
- 3) Double line to grd fault
- 4) One or two open conductor faults

Since any symmetrical fault causes unbalanced currents to flow in the s/m, the unsymmetrical faults are analyzed using symmetrical components.

Symmetrical Components

The analysis of unsymmetrical polyphase sys by the method of symmetrical components was introduced by Dr. C. Fortesque.


An unbalanced s/m of n related vectors can be resolved into n s/m of balanced vectors called symmetrical components of original vectors.

The n vectors of each set of components are equal in length and the phase angles b/w adjacent vectors of the set are equal.


In a 3 ϕ s/m, the three unbalanced vectors (either V_a, V_b, V_c or I_a, I_b & I_c) can be resolved into 3 balanced s/m of vectors. The vectors of the balanced s/m are called symmetrical components of the original s/m. The sym. components of 3 ϕ s/m are

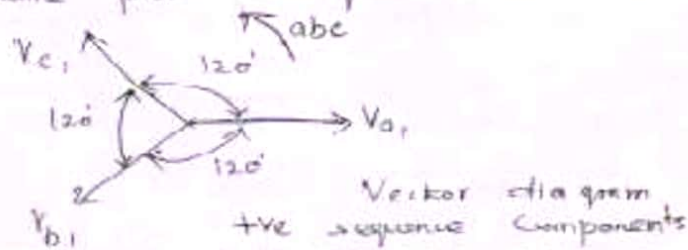- (i) Positive Sequence components
- (ii) Negative Sequence components
- (iii) Zero Sequence components


* The Positive sequence components consists of 3 vectors equal in magnitude, displaced from each other by 120° in phase, & having the same phase sequence as the original vectors.



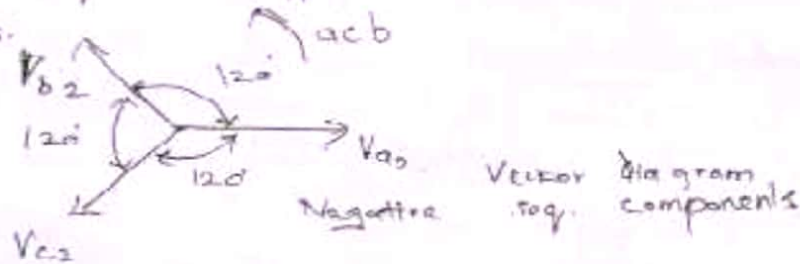* The negative sequence components consists of three vectors equal in magnitude, displaced from each other by 120° in phase, and having the phase sequence opposite to that of the original vectors.



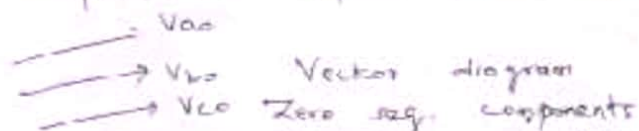* The zero sequence components consists of three vectors equal in magnitude and with zero phase displacement from each other.



Let V_a, V_b, V_c be the set of unbalanced voltage vectors with phase sequence abc. Each voltage vector can be resolved into positive, negative and zero sequence components.

Let $V_{a1}, V_{b1}, V_{c1} \rightarrow$ +ve seq. components of V_a, V_b, V_c resp. with phase sequence abc.

$V_{a2}, V_{b2}, V_{c2} \rightarrow$ -ve seq comp of V_a, V_b, V_c resp. with phase sequence acb

$V_{a0}, V_{b0}, V_{c0} \rightarrow$ Zero seq. components of V_a, V_b, V_c resp.

From the vector diagrams 3b sym. components of the following conclusion can be made.

1) On rotating the vector V_{a1} by 120° in anticlockwise direction we get V_{c1} .

2) On rotating the vector V_{a1} by 240° in anticlockwise direction we get V_{b1} .

3) On rotating V_{a2} by $120^\circ \rightarrow \text{anti} \rightarrow V_{a2}$

4) " " V_{a2} " 240° " $\rightarrow V_{c2}$

We can define an operator which causes a rotation of 120° in the anticlockwise direction, such an operator is denoted by the letter 'a'.

$$a = 1 \angle 120^\circ = 1 e^{+j2\pi/3} = \cos \frac{2\pi}{3} + j \sin \frac{2\pi}{3} \\ = -0.5 + j0.866$$

$$a^2 = 1 \angle 240^\circ = -0.5 - j0.866$$

$$a^3 = 1 \angle 360^\circ = 1$$

$$1 + a + a^2 = 1 + (-0.5 + j0.866) + (-0.5 - j0.866) \\ = 0$$

Computation of Unbalanced vectors from their symmetrical components.

Each of the original vector is the sum of its positive, negative and zero sequence components. Therefore the original unbalanced three phase voltage vectors can be expressed in terms of their components as shown below.

$$V_a = V_{a0} + V_{a1} + V_{a2} \quad \dots \quad (1)$$

$$V_b = V_{b0} + V_{b1} + V_{b2} \quad \dots \quad (2)$$

$$V_c = V_{c0} + V_{c1} + V_{c2} \quad \dots \quad (3)$$

From the vector diagrams, we get the following relations b/w various symmetrical components.

$$V_{b0} = V_{a0} ; \quad V_{b1} = a^2 V_{a1} ; \quad V_{b2} = a V_{a2} \quad (4)$$

$$V_{c0} = V_{a0} ; \quad V_{c1} = a V_{a1} ; \quad V_{c2} = a^2 V_{a2} \quad (5)$$

Using eqns 4, 5, 6, the V eqns 1, 2, 3 can be written as

$$V_a = V_{a0} + V_{a1} + V_{a2} \quad \dots \quad (6)$$

$$V_b = V_{a0} + a^2 V_{a1} + a V_{a2} \quad \dots \quad (7)$$

$$V_c = V_{a0} + a V_{a1} + a^2 V_{a2} \quad \dots \quad (8)$$

In matrix form,

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} \quad \dots \quad (9)$$

The eqn 9 can be used to compute the unbalanced voltage vectors from the knowledge of sym. components.

Computation of sym. components of unbalanced vectors:

The matrix eqn 9 can be written in the vector notation as

$$V = A V_{sy} \quad \rightarrow (10)$$

where $V = \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$; $A = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$; $V_{sy} = \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix}$

∴ pre multiplying the eqn 10 by A^{-1}

$$A^{-1} V = A^{-1} A V_{sy}$$

$$V_{sy} = A^{-1} V \quad \rightarrow (11)$$

$$A^{-1} = \frac{\text{Adjoint of } A}{\text{Determinant of } A}$$

Determinant of A

Let $\Delta = \text{Determinant of } A$

$$\begin{aligned} \therefore \Delta &= \begin{vmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{vmatrix} = 1(a^4 - a^2) - 1(a^2 - a) + 1(a - a^2) \\ &= (a - a^2) + (a - a^2) + (a - a^2) \\ &= 3(a - a^2) \end{aligned}$$

Let Δ_{ij} = cofactor of A_{ij}

$$\left(\because a^4 = a^3 \cdot a = a \right. \\ \left. a^3 = 1 \right)$$

$$\therefore \Delta_{11} = a^4 - a^2 = a - a^2$$

$$\Delta_{12} = -(a^2 - a) = a - a^2$$

$$\Delta_{13} = (a - a^2)$$

$$\Delta_{21} = -(a^2 - a) = a - a^2$$

$$\Delta_{22} = a^2 - 1$$

$$\Delta_{32} = -(a-1) = 1-a$$

$$\Delta_{23} = -(a-1) = 1-a$$

$$\Delta_{33} = a^2 - 1$$

$$\Delta_{31} = a - a^2$$

$$\begin{aligned} \therefore A^{-1} &= \frac{1}{\Delta} \begin{bmatrix} \Delta_{11} & \Delta_{12} & \Delta_{13} \\ \Delta_{21} & \Delta_{22} & \Delta_{23} \\ \Delta_{31} & \Delta_{32} & \Delta_{33} \end{bmatrix}^T \\ &= \frac{1}{3(a-a^2)} \begin{bmatrix} a-a^2 & a-a^2 & a-a^2 \\ a-a^2 & a^2-1 & 1-a \\ a-a^2 & 1-a & a^2-1 \end{bmatrix} \\ &= \frac{a-a^2}{3(a-a^2)} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \frac{a^2-1}{a-a^2} & \frac{1-a}{a-a^2} \\ 1 & \frac{1-a}{a-a^2} & \frac{a^2-1}{a-a^2} \end{bmatrix} \rightarrow (12) \end{aligned}$$

$$\frac{a^2-1}{a-a^2} = \frac{a^2-a^3}{a-a^2} = \frac{a(a-a^2)}{a-a^2} = a \rightarrow (13)$$

$$\frac{1-a}{a-a^2} = \frac{a^2(1-a)}{a^2(a-a^2)} = \frac{a^2(1-a)}{a^3-a^4} = \frac{a^2(1-a)}{1-a} = a^2 \rightarrow (14)$$

$$\therefore a^2 = 1 ; a^4 = a$$

Using eqn 13 & 14 $\rightarrow$ 12

$$A^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \rightarrow (15)$$

Sub eqn 15 in eqn 11

$$\begin{aligned} \Rightarrow V_{sy} &= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} V \\ \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} &= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} \rightarrow (16) \end{aligned}$$

The matrix eqn 16 can be expressed as three independent linear eqns as below.

$$V_{a0} = \frac{1}{3} (V_a + V_b + V_c) \rightarrow (17)$$

$$V_{a1} = \frac{1}{3} (V_a + aV_b + a^2V_c) \rightarrow (18)$$

$$V_{a2} = \frac{1}{3} (V_a + a^2V_b + aV_c) \rightarrow (19)$$

These eqns can be used to compute the sym. components of the unbalanced voltages.

Symmetrical Components of unbalanced current Vectors :-


The sym. components of unbalanced ct vectors can be obtained by an analysis similar to that of voltage vectors.

Let $I_a, I_b, I_c \rightarrow$ Unbalanced ct vectors with phase sequence abc.


$I_{a1}, I_{b1}, I_{c1} \rightarrow$ +ve sequence components of I_a, I_b & I_c resp with phase sequence abc.

$I_{a2}, I_{b2}, I_{c2} \rightarrow$ -ve sequence components of I_a, I_b, I_c resp with phase sequence abc.

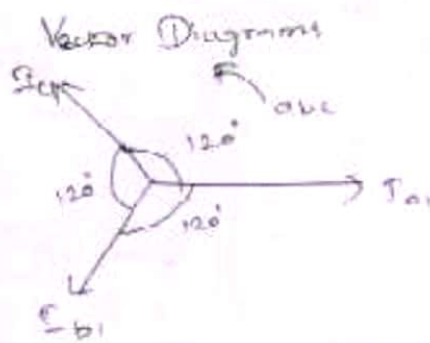
$I_{a0}, I_{b0}, I_{c0} \rightarrow$ Zero seq. components of I_a, I_b, I_c resp.



the seq. components

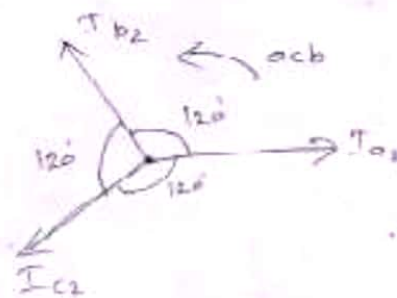

-ve seq. components

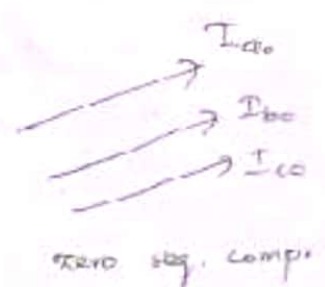

Vector diagrams of symmetrical components

of unbalanced 3-phase ct vectors

* The following eqns are used to compute the unbalanced ct vectors from knowledge of their sym. components. (Referring eqns 6, 7, 8)

$$I_a = I_{a0} + I_{a1} + I_{a2} \rightarrow A$$

$$I_b = I_{a0} + a^2 I_{a1} + a I_{a2} \rightarrow B$$

$$I_c = I_{a0} + a I_{a1} + a^2 I_{a2} \rightarrow C$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} \rightarrow T$$

* The following eqns are used to compute the symmetrical components of unbalanced current vectors.
(Referring eqn 14, 18, 19)

$$\begin{aligned} I_{a0} &= \frac{1}{3} [I_a + I_b + I_c] \rightarrow 0 \\ I_{a1} &= \frac{1}{3} [I_a + a I_b + a^2 I_c] \rightarrow E \\ I_{a2} &= \frac{1}{3} [I_a + a^2 I_b + a I_c] \rightarrow C \\ \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} &= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} \rightarrow \Pi \end{aligned}$$

Pbm The voltages across a 2 ϕ unbalanced load are
 $V_a = 300 \angle 20^\circ \text{ V}$, $V_b = 360 \angle 90^\circ \text{ V}$ & $V_c = 500 \angle -140^\circ \text{ V}$.
Determine the sym. components of voltages. Phasor seq. is abc

Soln The sym. components of V_a are given by

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

$$\therefore V_{a0} = \frac{1}{3} (V_a + V_b + V_c) \quad ; \quad V_{a1} = \frac{1}{3} (V_a + a V_b + a^2 V_c)$$

$$V_{a2} = \frac{1}{3} (V_a + a^2 V_b + a V_c)$$

$$\text{Given that } V_a = 300 \angle 20^\circ \text{ V} = 281.91 + j102.61 \text{ V}$$

$$V_b = 360 \angle 90^\circ \text{ V} = 0 + j360 \text{ V}$$

$$V_c = 500 \angle -140^\circ \text{ V} = -383.02 - j321.39 \text{ V}$$

$$\therefore a V_b = 1 \angle 120^\circ \times 360 \angle 90^\circ = 360 \angle 210^\circ = -311.77 - j180 \text{ V}$$

$$a^2 V_b = 1 \angle 240^\circ \times 360 \angle 90^\circ = 360 \angle 330^\circ = 311.77 - j180 \text{ V}$$

$$a V_c = 1 \angle 120^\circ \times 500 \angle -140^\circ = 500 \angle -20^\circ = 469.85 - j171.01 \text{ V}$$

$$a^2 V_c = 1 \angle 240^\circ \times 500 \angle -140^\circ = 500 \angle 100^\circ = -86.82 + j492.4 \text{ V}$$

$$\begin{aligned} V_{a0} &= \frac{1}{3} (V_a + V_b + V_c) = \frac{1}{3} (281.91 + j102.61 + j360 - 383.02 - j321.39) \\ &= -32.7 + j47.07 = 51.07 \angle 126^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} V_{a1} &= \frac{1}{3} (V_a + a V_b + a^2 V_c) = \frac{1}{3} (281.91 + j102.61 + (-311.77 - j180) - 86.82 + j492.4) \\ &= -38.89 + j138.34 = 143.7 \angle 106^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} V_{a2} &= \frac{1}{3} (V_a + a^2 V_b + a V_c) = \frac{1}{3} (281.91 + j102.61 + 311.77 - j180 + 469.85 - j171.01) \\ &= 354.51 - j129.2 = 364.05 \angle -12^\circ \text{ V} \end{aligned}$$

* We know that $V_{a0} = V_{b0} = V_{c0}$

∴ The zero sequence components are

$$V_{a0} = V_{b0} = V_{c0} = 57.89 \angle 120^\circ \text{ V}$$

* W.k. that $V_{b1} = a^2 V_{a1}$; $V_{c1} = a V_{a1}$

$$= 1 \angle 240^\circ \times 143.7 \angle 106^\circ$$

$$= 143.7 \angle 346^\circ \text{ V}$$

$$= 1 \angle 120^\circ \times 143.7 \angle 106^\circ$$

$$= 143.7 \angle 226^\circ \text{ V}$$

* W.k. that

$$V_{b2} = a V_{a2}$$

$$= 1 \angle 120^\circ \times 364.05 \angle 12^\circ$$

$$= 364.05 \angle 132^\circ \text{ V}$$

$$V_{c2} = a^2 V_{a2}$$

$$= 1 \angle 240^\circ \times 364.05 \angle 12^\circ$$

$$= 364.05 \angle 252^\circ \text{ V}$$

Prob

The symmetrical components of phase a voltages in a 3φ unbalanced sm are $V_{a0} = 10 \angle 180^\circ \text{ V}$, $V_{a1} = 50 \angle 0^\circ$ &

$V_{a2} = 20 \angle 90^\circ \text{ V}$. Determine phase voltages V_a, V_b & V_c .

The phase voltages of V_a, V_b, V_c are given by

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix}$$

$$V_a = V_{a0} + V_{a1} + V_{a2}$$

$$V_b = V_{a0} + a^2 V_{a1} + a V_{a2}$$

$$V_c = V_{a0} + a V_{a1} + a^2 V_{a2}$$

$$V_{a0} = 10 \angle 180^\circ = -10 \angle 0^\circ$$

$$V_{a1} = 50 \angle 0^\circ = 50 + j0$$

$$V_{a2} = 20 \angle 90^\circ = 0 + j20$$

$$a V_{a1} = 1 \angle 120^\circ \times 50 \angle 0^\circ = 50 \angle 120^\circ = -25 + j43.3$$

$$a^2 V_{a1} = 1 \angle 240^\circ \times 50 \angle 0^\circ = 50 \angle 240^\circ = -25 - j43.3$$

$$a V_{a2} = 1 \angle 120^\circ \times 20 \angle 90^\circ = 20 \angle 210^\circ = -17.32 - j10$$

$$a^2 V_{a2} = 1 \angle 240^\circ \times 20 \angle 90^\circ = 20 \angle 330^\circ = 17.32 - j10$$

$$V_a = V_{a0} + V_{a1} + V_{a2} = -10 + 50 + j0 + j20 = 40 + j20 = 44.72 \angle 26.5^\circ \text{ V}$$

$$V_b = V_{a0} + a^2 V_{a1} + a V_{a2} = -10 - 25 - j43.3 + (-17.32 - j10) = -52.32 - j53.3 = 74.69 \angle -134^\circ \text{ V}$$

$$V_c = V_{a0} + a V_{a1} + a^2 V_{a2} = -10 - 25 + j43.3 + 17.32 - j10 = -17.68 + j33.3 = 37.7 \angle 118^\circ \text{ V}$$

Prob The sym. components of phase a fault current in a 3φ unbalanced sm are $I_{a0} = 350 \angle 90^\circ \text{ A}$, $I_{a1} = 600 \angle -90^\circ \text{ A}$

& $I_{a2} = 250 \angle 90^\circ \text{ A}$. Determine the phase currents I_a, I_b & I_c .

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

(9)

$$I_a = I_{a0} + I_{a1} + I_{a2} = 0$$

$$I_b = I_{a0} + a^2 I_{a1} + a I_{a2} = j350 - 519.62 + j200 - 216.51$$

$$= -786.13 + j525 = 904.16 \angle 145^\circ \text{ A}$$

$$I_c = I_{a0} + a I_{a1} + a^2 I_{a2} = j350 + 519.62 + j200 + 216.51$$

$$= 736.13 + j525 = 904.16 \angle 35^\circ \text{ A}$$

Pbm

Determine the sym. components of the unbalanced set
 of $I_a = 10 \angle 0^\circ \text{ A}$, $I_b = 12 \angle 230^\circ \text{ A}$, $I_c = 10 \angle 130^\circ \text{ A}$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$I_{a0} = \frac{1}{3} (I_a + I_b + I_c) = \frac{1}{3} (10 - 7.71 - j9.19 - 6.43 + j7.66)$$

$$= -1.38 - j0.51 = 1.47 \angle -160^\circ$$

$$I_{a1} = \frac{1}{3} (I_a + a I_b + a^2 I_c) = \frac{1}{3} (10 + 11.82 - j2.08 + 9.35 + j1.74)$$

$$= 10.56 - j0.11 = 10.56 \angle -0.6^\circ = 10.56 \angle 10^\circ$$

$$I_{a2} = \frac{1}{3} (I_a + a^2 I_b + a I_c) = \frac{1}{3} (10 - 4.10 - j11.28 - 3.42 - j9.4)$$

$$= \frac{1}{3} (2.48 - j11.88)$$

$$= -0.83 - j3.96$$

$$= 4.04 \angle 137^\circ \text{ V}$$

h.k. that

$$I_{a0} = I_{b0} = I_{c0} = 1.47 \angle -160^\circ \text{ A}$$

$$I_{b1} = a^2 I_{a1} = 10.56 \angle 24^\circ \text{ A}, \quad I_{c1} = a I_{a1} = 10.56 \angle 120^\circ \text{ A}$$

$$I_{b2} = a I_{a2} = 10.56 \angle 157^\circ \text{ A}$$

$$I_{c2} = a^2 I_{a2} = 10.56 \angle 27^\circ \text{ A}$$

$$I_{c1} = a I_{a1} = 10.56 \angle 120^\circ \text{ A}$$

Sequence Impedances Z_1 Seq. n/w s

— are useful in the analysis of unsymmetrical faults in the power s/m.

Sequence Impedances & Sequence Networks (10)

The sequence impedances are impedances offered by ckt elements (or power s/m components) to positive, negative & zero sequence currents.

In any element of a ckt, the voltage drop caused by current of a certain sequence depends on the impedance of the element to that sequence i.e. the sequence impedance.

The imp of a circuit element when positive sequence cts alone are flowing is called the the +ve seq. imp.

-ve seq. Impedance

When only negative seq. currents are present, the impedance is called negative seq. imp.

Zero seq. Imp.

When only zero seq. currents are present, the imp is called zero seq. imp.

The imp of any element of a balanced ckt to ~~the~~ it of one seq. may be different from imp to it of another seq.

Sequence Networks :-

The single phase equivalent ckt of power s/m (impedance or reactance diagram) formed using the impedances of any one sequence only is called the sequence n/w for that particular sequence.

+ve seq. n/w :

The impedance or reactance dia formed using positive sequence ~~the~~ impedance is called +ve seq. n/w.

-ve seq. n/w :

The impedance or reactance dia formed using -ve seq. impedance is called -ve seq. n/w.

Zero Seq. n/w :

The impedance on reactance diagram formed using zero seq. impedance is called zero


seq. n/w.

In unsymmetrical fault analysis of a ps, the positive, negative and zero seq. n/w of the s/n are determined & then they are inter-connected to represent the various unbalanced fault conditions.

Each seq. n/w includes the generated emfs and impedances of like seq. Also, the seq. n/w carries only the ct of like seq.

Sequence Impedances of n/w of Generator

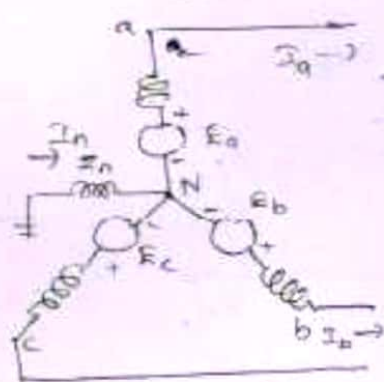Let consider the 2 ϕ equivalent ckt of a (G)



The neutral of the (G) is grounded through a reactance, Z_n .

When the (G) is delivering a balanced load or under sym. fault the neutral ct is zero.

But when the (G) is delivering an unbalanced load or during unsym. faults the neutral ct flows through Z_n .

3 ϕ equr ckt of a (G) grounded through a reactance.

The (G) is designed to supply balanced 3 ϕ voltages.

$\therefore$ The generated emfs are of +ve seq. only.

Let E_a, E_b, E_c be generated emf per phase in phase a, b, c resp. (positive seq. emf)

Z_1 = +ve seq. imp per phase of (G)

Z_2 = -ve "

Z_0 = zero "


Z_n = Neutral reactance

Z_0 = Total zero seq. imp per phase of zero seq. n/w of (G)


- The positive seq. n/w consists of an emf ⁽¹²⁾ in series with +ve seq. imp of the (51).
- ⇒ The negative & zero seq. n/w will not have any sources but include their respective seq. imp.

The positive, -ve & zero seq. ct paths seq. n/ws :-


(a) +ve seq. ct paths

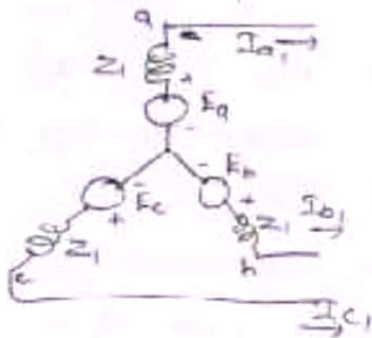


-ve seq. ct paths

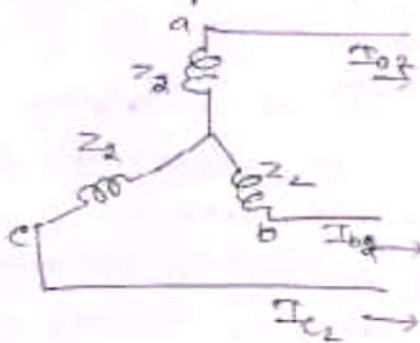


zero seq. ct paths

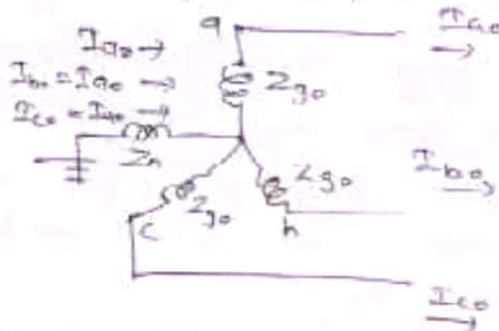


+ve seq. n/w

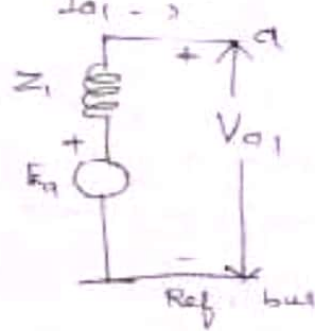

-ve seq. n/w

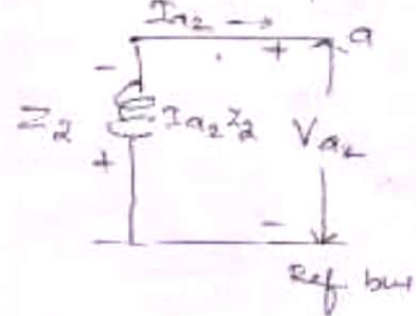

Zero seq. n/w

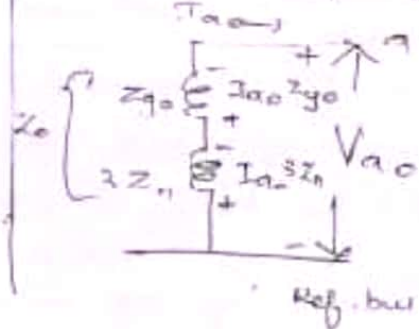

The reactances in +ve seq. n/w is subtransient, transient or syn. reactance depending on whether subtransient, transient or steady state conditions are being studied.

(13)
Under no load condition, the only E_a is the induced emf per phase.

Under load or fault condition E_a is replaced by E_a' for subtransient state $E_a \Rightarrow E_a'$,
for transient state $E_a \Rightarrow E_a''$.

The +ve Σ_1 -ve seq cts are balanced cts and cto. they will not pass through neutral wireline.

Zero seq n/w:

The ct through neutral wireline is $3I_{a0}$.
The zero seq. voltage drop from point a to gnd is $-3I_{a0}Z_n - I_{a0}Z_{g0}$.

The zero seq n/w is a single phase n/w & assumed to carry only the zero seq ct of one phase. Hence the zero seq ct of one phase, must have an imp. of $3Z_n + Z_{g0}$.

$\therefore$ Total zero seq. imp per phase of a } $Z_0 = 3Z_n + Z_{g0}$
reactance

(14) grounded through



From fig, eqns for phase - a component voltages are

$$V_{a1} = E_a - I_{a1}Z_1$$

$$V_{a2} = -I_{a2}Z_2$$

$$V_{a0} = -I_{a0}Z_0$$

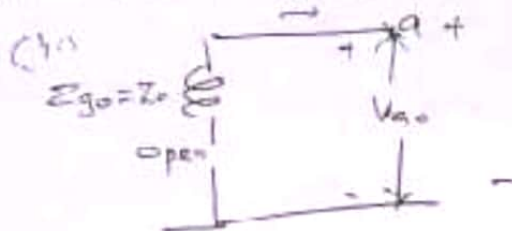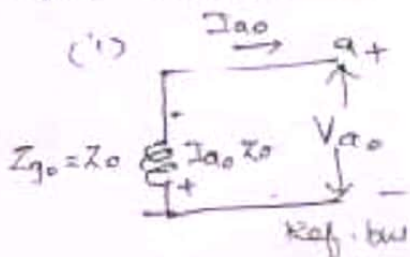The zero seq n/w of (14) when the neutral is solidly grounded (i.e. directly grounded) & when the neutral is ungrounded are (15) resp.



In these cases there is no change in +ve Σ_1 -ve seq. n/w.

(11)
The seq. rms of syn. (M) is same as that of generator when the directions of cts in the seq. rms of (9) are reversed.

Sequence Imps Z_1 rms of Tr. line:

The imp. per phase of tr. line for balanced cts are independent of phase sequence. This is due to the transposed tr. lines. Therefore, the impedances offered by the ~~symmetry~~ tr. lines for positive & negative sequence cts are identical.

The zero seq. ct is identical (both in mag & phase) in each phase conductor & returns through the grd, through overhead grd wires or through both.

The grd wires being grounded at several towers, the return cts in the ground wire may not be uniform along the entire length of tr. line.

But for +ve & -ve seq. cts there is no return ct & they have a phase diff of 120° . $\therefore$ The magnetic field due to zero seq. ct is different from the mag. field caused by either +ve or -ve seq. ct.




Due to difference in the mag. field, the zero sequence inductive reactance is 2 to 3 times the +ve seq. reactance.

Let $Z_1 \rightarrow$ +ve seq. imp of tr. line

$Z_2 \rightarrow$ -ve "

$Z_0 \rightarrow$ Zero "

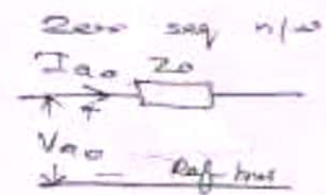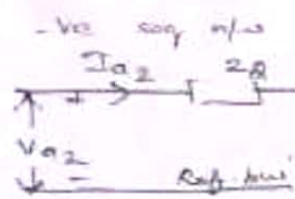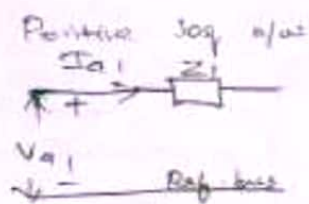The +ve, -ve & zero ⁽¹⁵⁾ seq. impedances of a linear are represented as a series impedance on their respective sequence n/w's.



Sequence Impedances of n/w's of T/f :

When the applied voltage is balanced, the +ve & -ve seq. of linear, symmetrical, static devices are identical.



$\therefore$ in a t/f the +ve & -ve seq. imp are identical.

Even though the zero seq. imp may slightly differ from +ve & -ve seq. imp., it is normal to assume the zero seq. imp. as equal to +ve or -ve seq. imp.


When the neutral of star connection is grounded through reactance Z_n then $3Z_n$ should be added to zero seq. imp of t/f to get the total zero impedance.

Let $Z_1 \rightarrow$ +ve seq. imp of t/f
 $Z_2 \rightarrow$ -ve "
 $Z_0 \rightarrow$ zero "

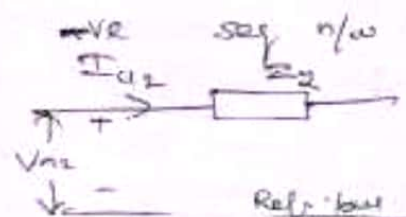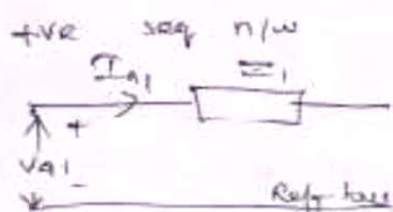The +ve, -ve seq. imp's of t/f are represented as a series impedance in their respective seq. n/w



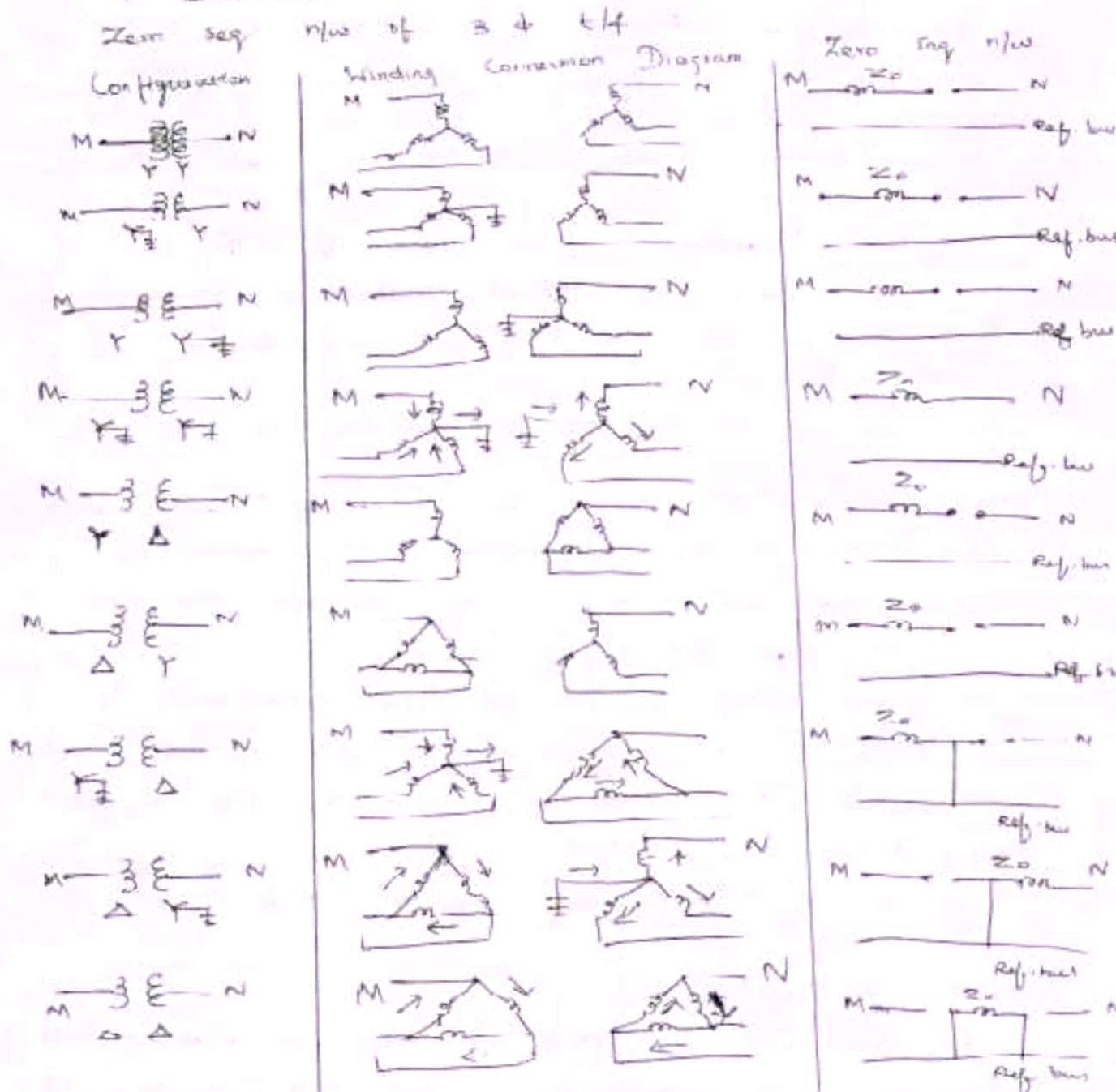The zero seq n/w of the $\frac{E}{f}$ depends on type of connections (Y or Δ) of the primary & sec wdg of $\frac{E}{f}$ & also on the grounding of neutral in Y connection.



The arrows on the wdg indicate path for zero seq. & the absence of arrows indicate that there is no path for zero seq. wdg.

→ When magnetizing it is neglected the pry wdg will carry it only if there is a ct flow on the secondary wdg. $\therefore$ The zero seq. ct can flow in the pry wdg of a $\frac{E}{f}$ only if there is a path for zero seq. ct in sec wdg on vice-versa.

→ If the neutral pt in the γ connected wdg is not grounded then there is no path for zero seq. It in γ connected wdg.



→ The zero seq. ckt flows in the star connected wdg & in the lines connected to the wdg only when the neutral pt is grounded.

→ The zero seq. it can circulate in the delta connected wdg but the zero seq. it can't flow through the lines connected to the delta connected wdg.

Sequence Imps & N/ws of Loads
In-balanced γ or Δ connected loads the positive, negative & zero seq. impedances are equal.
When the neutral pt of star connected load is grounded through a reactance Z_n then $3Z_n$ is added to the zero seq. imp. to get the total zero seq. imp of load.

Let $Z_{L1} \rightarrow +ve$ seq. imp of load
 $Z_{L2} \rightarrow -ve$ "
 $Z_{L0} \rightarrow zero$ "

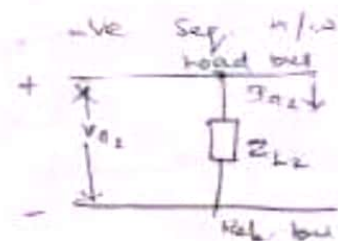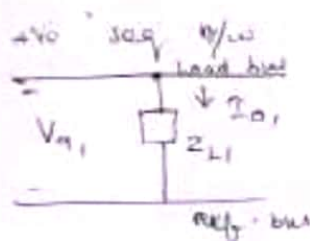+ve & -ve seq. imp. of load are represented as a shunt imp. in their respective seq. n/w.



The zero seq. n/w of the 3- ϕ load depends on the type of connection, i.e. γ or Δ connection. The zero seq. it will flow in n/w only if a return path exists for it.

18

Diagram 1: A load Z_{L0} is connected to a top bus. The reference bus is below.

Diagram 2: A load Z_{L0} is connected to a top bus. The reference bus is below.




Diagram 3: A load Z_{L0} is connected to a top bus. The reference bus is below.

Diagram 4: A load Z_{L0} is connected to a top bus. The reference bus is below.


Diagram 5: A load Z_{L0} is connected to a top bus. The reference bus is below.

Let	$X_{G1} \rightarrow$	the seq.	Response of	Gen. G1
	$X_{M1} \rightarrow$	"	"	Motor M
	$X_{T1,1} \rightarrow$	"	"	T/f T ₁
	$X_{T2,1} \rightarrow$	"	"	T/f T ₂
	$X_{T3,1} \rightarrow$	"	"	T/f T ₃
	$X_{T4,1} \rightarrow$	"	"	T ₃ line 1
	$X_{T3,2} \rightarrow$	"	"	T ₃ line 2

(19)

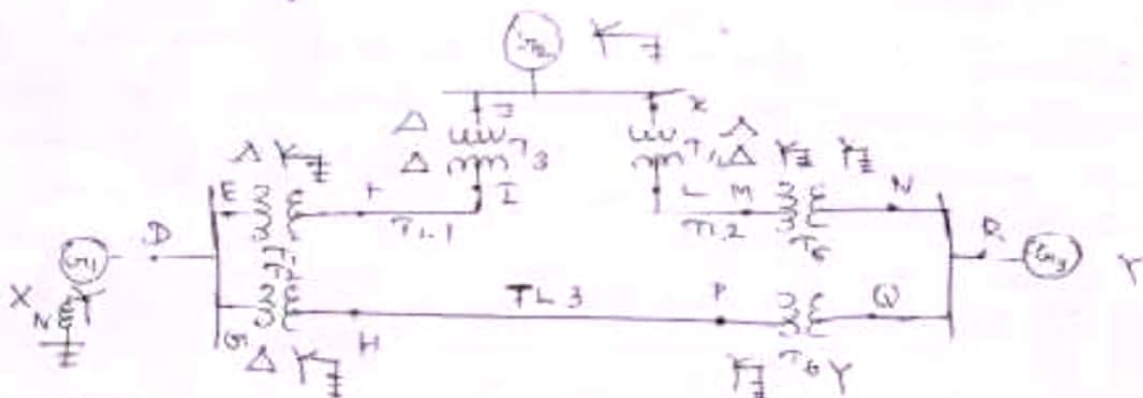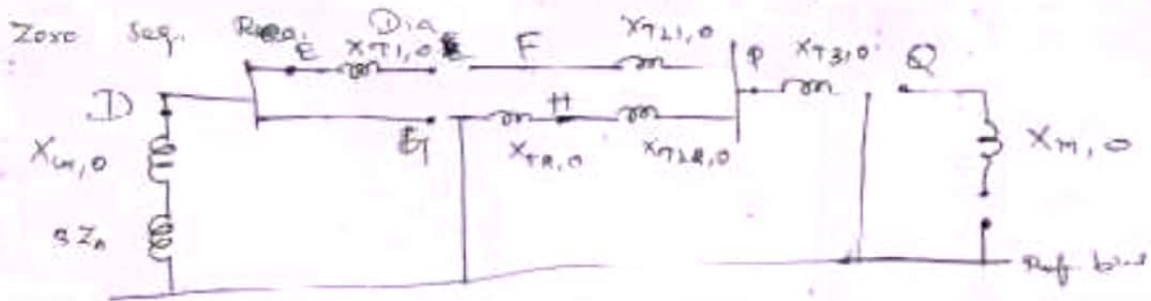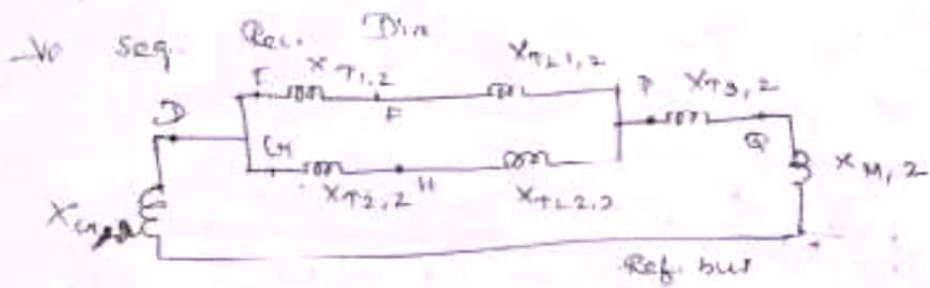


Draw +ve. seq. zero seq. Rec. Dia

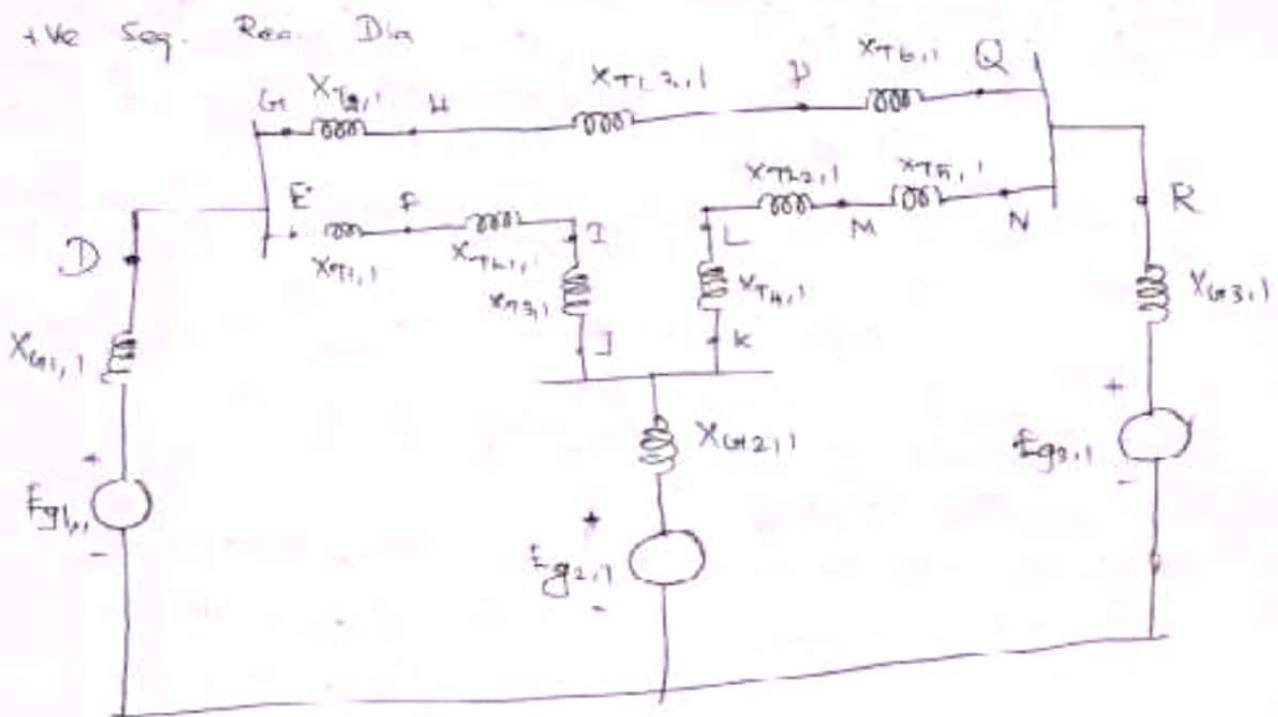



Zero Jeq Rao Dia

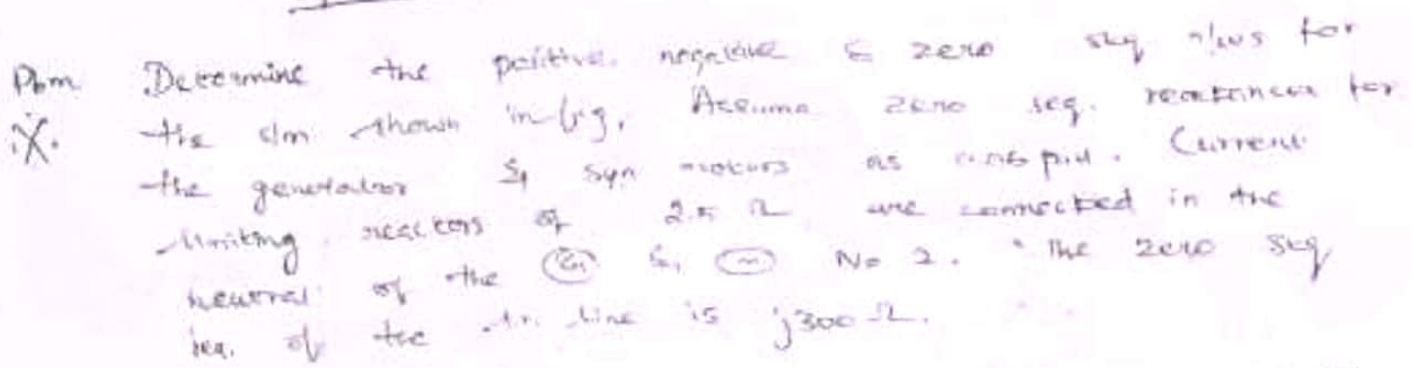

Base voltage $V_{b, \text{new}} = 11 \text{ kV}$.

Does not change.

NEGATIVE

Zero

$$X_{G,0} = 0.06 \text{ p.u.}$$

$$X_{\text{un}} = \frac{\text{Actual Neutral Reactance}}{\text{Base Impedance}}$$

Base Imp, $Z_0 = \frac{(KV_{b, \text{new}})^2}{MVA_{\text{new}}} = \frac{11^2}{25} = 4.84 \Omega$

(21)

$$\therefore X_{1,N} = \frac{2.5}{4.84} = 0.517 \text{ p.u.}$$

Seq. Reactance of T/f T_1 :-

$$\left. \begin{array}{l} \text{New p.u. reactance} \\ \text{of T/f } T_1 \end{array} \right\} = X_{p,old} \times \left(\frac{KV_{b,old}}{KV_{b,new}} \right)^2 \times \frac{MVA_{b,new}}{MVA_{b,old}}$$

$$\text{Here } X_{p,old} = 0.1 = 0.1 \text{ p.u.}$$

$$KV_{b,old} = 11 \text{ kV}$$

$$KV_{b,old} = 10.8 \text{ kV}$$

$$MVA_{b,new} = 25 \text{ MVA}$$

$$MVA_{b,old} = 3 \text{ MVA}$$

$$\therefore \text{New p.u. Reactance of T/f } T_1 = 0.1 \times \left(\frac{10.8}{11} \right)^2 \times \left(\frac{25}{3} \right) = 0.08 \text{ p.u.}$$

$\Rightarrow$ In t/f the specified reactance is the seq. reactance. Also we assume that the +ve, -ve & zero seq. reactance of the t/f are equal.

$$\therefore \text{+ve seq. Res. of T/f } T_1, X_{T_1,1} = 0.08 \text{ p.u.}$$

$$\text{-ve " " " } X_{T_1,2} = 0.08 \text{ p.u.}$$

$$\text{Zero " " " } X_{T_1,0} = 0.08 \text{ p.u.}$$

Seq. Res. of Tr. line :-

$$\left. \begin{array}{l} \text{The base kv on HT side} \\ \text{of t/f } T_1 \end{array} \right\} = \text{Base kv on LT side} \times \frac{\text{HT V Rating}}{\text{LT V Rating}}$$

$$= 11 \times \frac{121}{10.8} = 123.24 \text{ kV}$$

$$\text{New } KV_{b,new} = 123.24 \text{ kV}$$

$$\text{Base impedance} = \frac{(KV_{b,new})^2}{MVA_{b,new}} = \frac{123.24^2}{30} = 506.27 \Omega$$

$$\text{pu Reactance of Tr. line} = \frac{\text{Actual Reactance}}{\text{Base impedance}} = \frac{100}{506.27} = 0.198 \text{ p.u.}$$

$\Rightarrow$ The specified reactance in single line diagram is the seq. reactance. Also the negative sequence reactance of a tr. line is same as that of +ve seq. reactance.

(a3)
 $\therefore$ +ve seq. reactance of tr. line, $X_{TL1,1} = 0.188 \text{ pu}$
 $-ve$ " " " $X_{TL1,2} = 0.198 \text{ pu}$
 pu value of zero seq. react. of tr. line $X_{TL1,0} = \frac{\text{zero seq. react.}}{\text{Base imp}}$

$$= \frac{300}{500 \text{ MVA}} = 0.6 \text{ pu}$$

Seq. Reactance of T/f T₂:

The ratings of both connections of T/f T₁ & T₂ are identical & so the seq. reactances of

T₁ & T₂ are same.

+ve seq. react. of T/f T₂, $X_{T2,1} = 0.08 \text{ pu}$
 $-ve$ " " " $X_{T2,2} = 0.08 \text{ pu}$
 $Zero$ " " " $X_{T2,0} = 0.08 \text{ pu}$

Seq. React. of Syn (M) M₁

$$\left. \begin{array}{l} \text{Base kV on LT side} \\ \text{of T/f T}_2 \end{array} \right\} = \text{Base kV on HT side} \times \frac{\text{LT V. Rating}}{\text{HT V. Rating}}$$

$$= 123.24 \times \frac{10.8}{121} = 11 \text{ kV}$$

$$\therefore kV_{b, \text{new}} = 11 \text{ kV}$$

$$\text{New pu React. of M, M}_1 = X_{\text{pu old}} \times \left(\frac{kV_{\text{old}}}{kV_{b, \text{new}}} \right)^2 \times \frac{MVA_{b, \text{old}}}{MVA_{b, \text{new}}}$$

$$= 0.125 \times \left(\frac{10}{11} \right)^2 \times \left(\frac{25}{15} \right)$$

$$= 0.344 \text{ pu}$$

$\therefore$ The react. specified in single line dia is +ve seq. reactance. Also the -ve seq react. of syn. (M) is same as that of +ve seq. react.

$\therefore$ +ve seq. Reactance of M, M₁, $X_{M1,1} = 0.344 \text{ pu}$
 $-ve$ " " " $X_{M1,2} = 0.344 \text{ pu}$
 $Zero$ " " " $X_{M1,0} = 0.002 \text{ pu}$

$$\left. \begin{array}{l} \text{Zero seq. react. of } \textcircled{M}, M_1 \text{ on} \\ \text{new bases} \end{array} \right\} X_{M1,0} = X_{\text{pu old}} \times \left(\frac{kV_{\text{old}}}{kV_{b, \text{new}}} \right)^2 \times \frac{MVA_{b, \text{old}}}{MVA_{b, \text{new}}}$$

$$= 0.06 \times \left(\frac{10}{11} \right)^2 \times \left(\frac{25}{15} \right)$$

$$= 0.003 \text{ pu}$$

Seq. Res. of sym (M) M2:

$$\text{New p.u. Res. of (M) } M_2 = X_{p.u. old} \left(\frac{KV_{b,old}}{KV_{b,new}} \right)^2 \times \frac{MVA_{b,new}}{MVA_{b,old}}$$

$$\text{Hence } X_1 = 0.25 \times \left(\frac{10}{11} \right)^2 \times \left(\frac{25}{7.5} \right) = 0.689 \text{ p.u.}$$

+ve seq. Res. of (M) M2, $X_{M2,1} = 0.689 \text{ p.u.}$


-ve " " $X_{M2,2} = 0.689 \text{ p.u.}$

The zero seq. resistance of (M) M1, only the new buses, $X_{M2,0} = X_{p.u. old} \left(\frac{KV_{b,old}}{KV_{b,new}} \right)^2 \times \frac{MVA_{b,new}}{MVA_{b,old}}$

$$= 0.16 \times \left(\frac{10}{11} \right)^2 \times \left(\frac{25}{7.5} \right) = 0.165 \text{ p.u.}$$


p.u. value of (M) neutral reactance $X_{MN} = \frac{\text{Actual neutral Res.}}{\text{Base imp}}$
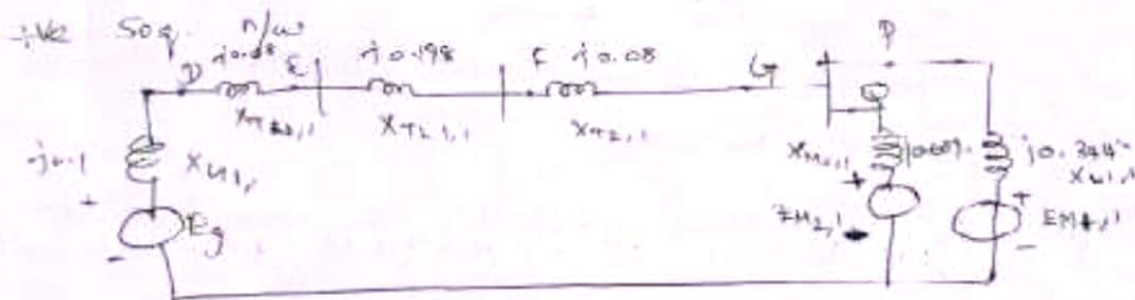
$$= \frac{2\pi}{4.04} = 0.151 \text{ p.u.}$$



-ve Seq. n/w
Same as +ve seq. n/w (-ve sources $E_1, E_{M1,1}, E_{M2,1}$)

Zero seq. n/w

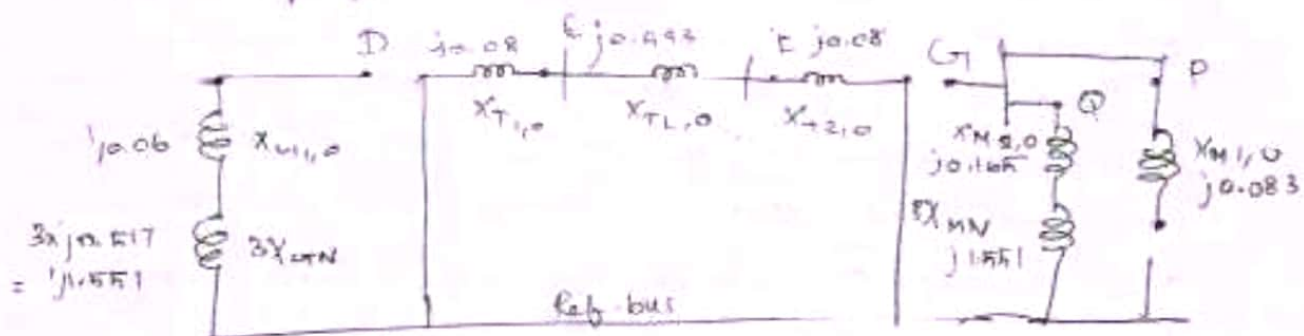

Unsymmetrical Fault Analysis

When the r/w is unsymmetrically faulted or loaded, neither the phase cts nor the phase voltages will possess three phase symmetry.

Most of the slm faults are unsymmetrical faults. It consists of unsym. short ckt fault or unsym. fault through impedance, or open conductor faults. If the insulation of the slm fails at any pt or if a conducting object comes in contact with a bare conductor, an unsym. short ckt fault is said to occur.

If unsym. fault occurs, the unbalanced cts will flow in the slm. We are using sym. components to analyse unsym. faults.

To determine positive & negative and zero seq. impedance, we can use Thevenin's theorem on Bus impedance matrix.

Types of unsymmetrical faults: The unsym. faults are the faults in which the fault cts in the three phases are unequal.

Types:

- * Single line to ground fault (L-G)
- * Line to line fault (L-L)
- * Double line to ground fault (L-L-G)
- * Open conductor faults.

Causes:-
Lightning; wind damage, line falling across lines, vehicles colliding with towers or poles, birds shorting lines, breakers due to excessive line loading or snow loading, salt spray.

Short ckt analysis of unbalanced low order systems:-


1. Draw the +ve, -ve & zero seq. r/w's with their appropriate description.

2. (phase of type of fault (L-L, L-L or L-L-g) & location of fault & mathematical description for the particular type of fault.

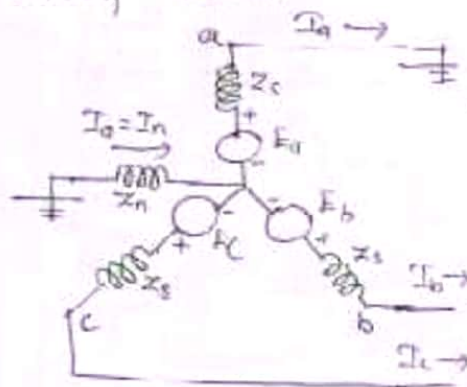3. Using Thevenin's theorem or bus impedance matrix determine the solution of the Y_{bus} eqns.
Fault I_f , post fault ckt , post fault voltages, are found at the point of fault,
all the bus voltages & the line flows.

Single Line to Ground fault on an unloaded Generator

The most common type fault, single line to ground fault is caused by lightning or by conductors making contact with grounded structures.



The ckt dia shows a single line to ground fault on an unloaded γ (star) connected $\odot$ with its neutral grounded through a reactance Z_n .

Assuming fault occurs on phase 'a',



Now the fault ckt , $I_f = I_a$

Since the generator is unloaded the ct in other phases are zero.

The condition at the fault is expressed by the following eqns

$$I_b = 0 ; I_c = 0 ; V_a = 0 ;$$

The sym. components of the currents are

gn by

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} \rightarrow 1$$

On substituting the condition $I_b = I_c = 0$ in the sym. components of eq. we get

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ 0 \\ 0 \end{bmatrix}$$

$$I_{a0} = \frac{1}{3} I_a ; I_{a1} = \frac{1}{3} I_a ; I_{a2} = \frac{1}{3} I_a$$

$$\therefore I_{a0} = I_{a1} = I_{a2} = \frac{I_a}{3} \rightarrow 2$$

From the seq. eqs of the (4) we get the following matrix eqn

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 0 \\ E_a \\ 0 \end{bmatrix} - \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

On sub $I_{a0} = I_{a1}$ & $I_{a2} = I_{a1}$

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 0 \\ E_a \\ 0 \end{bmatrix} - \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix} \begin{bmatrix} I_{a1} \\ I_{a1} \\ I_{a1} \end{bmatrix}$$

$$V_{a0} = -Z_0 I_{a1} \rightarrow A$$

$$V_{a1} = \frac{E_a}{3} - Z_1 I_{a1} \rightarrow B$$

$$V_{a2} = -Z_2 I_{a1} \rightarrow C$$

On adding eqns A, B, C

$$V_{a0} + V_{a1} + V_{a2} = -I_{a1} Z_0 + \frac{E_a}{3} - Z_1 I_{a1} - Z_2 I_{a1} \rightarrow D$$

Single phase ~~to~~ a is shorted to gnd, $\therefore$


$$V_a = V_{a0} + V_{a1} + V_{a2} = 0 \quad \therefore \text{eqn D can be written as}$$

$$-I_{a1} Z_0 + \frac{E_a}{3} - I_{a1} Z_1 - I_{a1} Z_2 = 0$$

$$I_{a1} = \frac{E_a}{Z_0 + Z_1 + Z_2}$$

Using this eqn the eqn set of (4) during single line to ground fault is drawn as shown in fig.

(2)

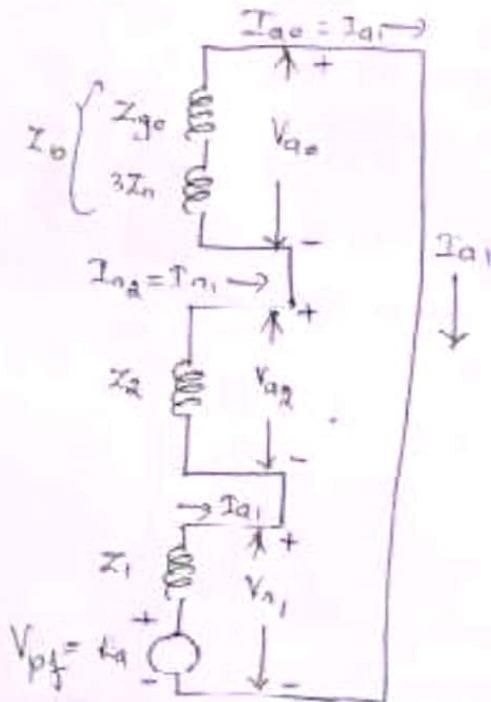

Connection of sequence net of an unloaded (or) for line to ground fault on phase - a.

Here the +ve, -ve E_a zero seq n/w of the (a) are connected in series.

If the neutral of the (G) is not grounded, the zero seq net is open-circuited & Z_0 is infinite.

Under this condition

I_{a1} is zero & so I_{a2} & I_{a0} must be zero. $\therefore$ no path exists for the flow of it in the fault unless the (G) neutral is grounded.

Here the fault is gn by

Seqs are gn by
$$I_f = I_{a1} = 3 I_{a1}$$


$$I_{a1} = I_{a2} = I_{a0} = \frac{I_f}{3}$$

$$I_{a1} = \frac{V_{pf}}{Z_1 + Z_2 + Z_0}$$

Single line to ground fault through an impedance

There may be situations in which the fault path includes an impedance b/w the faulted points. In these situations, the fault impedances are included at appropriate points in the ckt obtained by connecting seq. n/w.

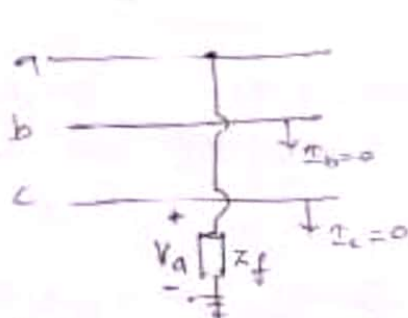Let a single line to ground fault at point F in a p.s. through a fault impedance Z_f can be represented by connecting two skels as shown in fig.



At fault pt F, the following relations must exist

$$\left. \begin{aligned} I_b &= 0, \quad I_c = 0 \\ V_a &= Z_f I_a \end{aligned} \right\} \rightarrow (1)$$

The sym. components of the fault ct are

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ 0 \\ 0 \end{bmatrix}$$

$$\therefore I_{a0} = I_{a2} = I_{a1} = \frac{I_a}{3} \rightarrow (2)$$

$$\text{or } I_a = 3 I_{a1} \rightarrow (3)$$


Expressing the voltage V_a in terms of sym. components we have $V_a = V_{a1} + V_{a2} + V_{a0} \rightarrow (4)$

Use eqn (1) & (3)

$$\Rightarrow V_a = Z_f I_a = 3 Z_f I_{a1} = V_{a1} + V_{a2} + V_{a0}$$

From eqn 2 & 3, all sequence cts are equal & the sum of sequence voltages equals $3 Z_f I_{a1}$.

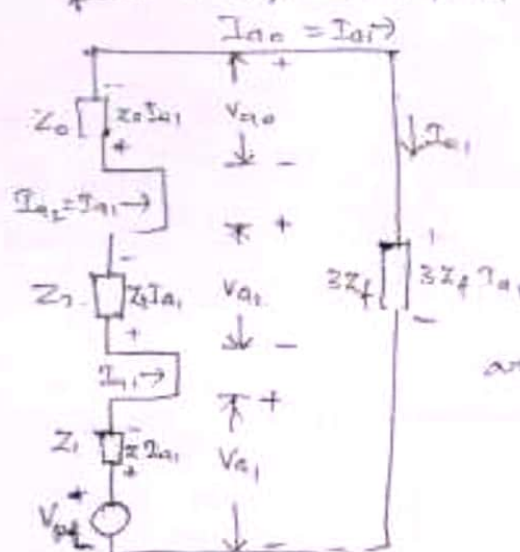connection of seq. cts for a single line to gnd fault through an imp. Z_f



Phase voltages are given by

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix}$$

From fig,

$$I_{a1} = \frac{V_{pf}}{(Z_1 + Z_2 + Z_0) + 3Z_f} \rightarrow (6)$$

$$\text{Fault ct } I_f = I_a = 3 I_{a1}$$

$$= \frac{3 V_{pf}}{(Z_1 + Z_2 + Z_0) + 3Z_f} \rightarrow (7)$$

Sym. components of phase a voltages are calculated by writing KVL

$$V_{a1} = V_{pf} - Z_1 I_{a1}$$

$$V_{a2} = -Z_2 I_{a1}$$


$$V_{a0} = -Z_0 I_{a1}$$

(29)

Line to Line Fault of an unloaded (29)

Let consider phase b & phase c are shorted.

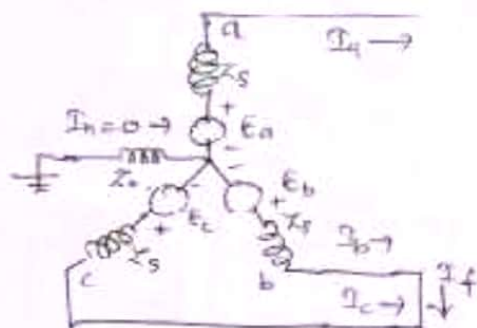The circuit diagram shows a line to line fault of an unloaded system.



Line to line fault

Now the fault is $I_f = I_b = -I_c$

Since the system is unloaded, the current in phase a is zero.

The conditions at the fault are expressed by the following eqns.

$$\left. \begin{aligned} V_b &= V_c & I_a &= 0 \\ I_b + I_c &= 0 \Rightarrow I_b = -I_c \end{aligned} \right\} \rightarrow 1$$

With $V_c = V_b$ the sym. components of voltages are given by

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} \rightarrow 2$$

$$V_{a0} = \frac{1}{3} (V_a + V_b + V_c)$$

$$V_{a1} = \frac{1}{3} (V_a + aV_b + a^2V_c) \rightarrow 3$$

$$V_{a2} = \frac{1}{3} (V_a + a^2V_b + aV_c) \rightarrow 4$$

From eqns 3 & 4 $\Rightarrow V_{a1} = V_{a2} \rightarrow 5$

The sym. components of currents are given by

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

10. sub $I_a = 0$; $I_b = -I_c$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ -I_c \\ I_c \end{bmatrix}$$

$$I_{a0} = \frac{1}{3} (-I_c + I_c) = 0$$

$$I_{a1} = \frac{1}{3} (-aI_c + a^2I_c) \rightarrow 6$$

$$I_{a2} = \frac{1}{3} (-a^2I_c + aI_c) \rightarrow 7$$

From eqn 6 & 7

$$I_{a2} = \frac{1}{3} (-a^2 I_c + a I_c) = -\frac{1}{3} (-a I_c + a^2 I_c)$$

from eqns 6 & 7

$$I_{a2} = -I_{a1} \rightarrow (8)$$

from the seq. n/ws of the (a) we get the following matrix eqns:

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \begin{bmatrix} 0 \\ E_a \\ 0 \end{bmatrix} - \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

On sub $I_{a0} = 0$; $I_{a2} = -I_{a1}$

$$\Rightarrow \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \begin{bmatrix} 0 \\ E_a \\ 0 \end{bmatrix} - \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix} \begin{bmatrix} 0 \\ I_{a1} \\ -I_{a1} \end{bmatrix}$$

$$V_{a0} = 0$$

$$V_{a1} = E_a - I_{a1} Z_1 \rightarrow (9)$$

$$V_{a2} = Z_2 I_{a1} \rightarrow (10)$$


From eqn 5 we know $V_{a1} = V_{a2}$

$$\therefore E_a - I_{a1} Z_1 = Z_2 I_{a1}$$

$$I_{a1} (Z_1 + Z_2) = E_a$$

$$\therefore I_{a1} = \frac{E_a}{Z_1 + Z_2}$$

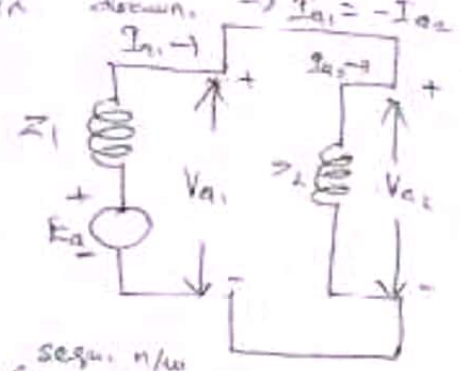this using eqn (8) & (9) & (10) of (a) during line to line fault in shown. $\rightarrow I_{a1} = -I_{a2}$



seq. n/w
(line to line fault
b/w phase b & c)

since $V_{a1} = V_{a2}$, here the +ve & -ve seq. n/w of the (a) must be in || el.

since $V_{a0} = 0$, then zero seq. n/w is shorted & so it need not be considered,

Since this type of fault does not involve ground, the neutral current $I_n = 0$.

Hence the presence or absence of grounded neutral at the fault does not affect the fault current.

Hence fault current,
$$I_f = I_b = -I_c$$

The unbalanced currents I_a, I_b & I_c are related to two sym. comp of cts are

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

$$I_b = I_{a0} + a^2 I_{a1} + a I_{a2}$$


On sub $I_{a0} = 0$ & $I_{a2} = -I_{a1}$

$$\Rightarrow I_b = a^2 I_{a1} - a I_{a1}$$

$$= I_{a1} (a^2 - a)$$

$$\therefore I_f = I_b = I_{a1} (a^2 - a)$$

Line to line fault through impedance:

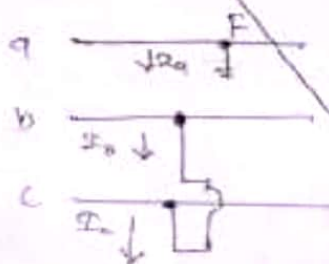

The following Relations exist at the fault


$$V_b = V_c ; I_a = 0 ; I_b = -I_c$$

The V & cts under this fault condition are same as that of a line-to-line fault on an ungrounded system.

Hence for a line to line fault


$$V_{a1} = V_{a2}$$

$$I_{a1} = \frac{V_{pf}}{Z_1 + Z_2}$$

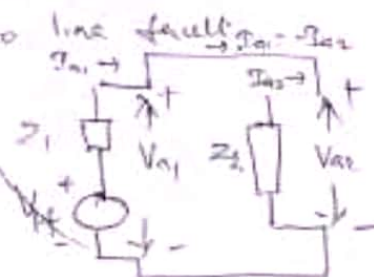

Fault through Impedance in line to line fault

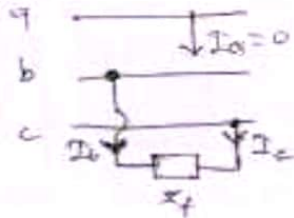A line to line fault at pt F in a 3 phase b & c through a fault imp Z_f can be represented by connecting three stubs as shown for



The cts E_i V_i at the fault can be expressed as

$$I_a = 0 ; I_b = -I_c$$

$$\text{Also } V_b - V_c = I_b Z_f \quad \rightarrow 1$$

$$V_c = V_b - I_b Z_f \quad \rightarrow 2$$

The sym comp of the cts after sub $I_c = 0$ & $I_c = -I_b$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ I_b \\ -I_b \end{bmatrix}$$

$$I_{a0} = \frac{1}{3} (I_b - I_b) = 0$$

$$I_{a1} = \frac{1}{3} (4I_b - a^2 I_b)$$

$$I_{a2} = \frac{1}{3} (a^2 I_b - a I_b) = -\frac{1}{3} (a I_b - a^2 I_b) = -I_{a1}$$

$$\therefore I_{a0} = 0 ; I_{a2} = -I_{a1} \quad \rightarrow 3$$

The line cts can be obtained from the matrix eqn after sub these conditions (3)

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 \\ I_{a1} \\ -I_{a1} \end{bmatrix}$$

$$I_b = (a^2 I_{a1} - a I_{a1}) = I_{a1} (a^2 - a) \quad \rightarrow (4)$$

$$= I_{a1} \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} + \frac{1}{2} - j\frac{\sqrt{3}}{2} \right) = -j\sqrt{3} I_{a1}$$

$$\text{or } = I_{a1} (-0.5 - j0.866 - (-0.5 + j0.866))$$

$$= I_{a1} (-0.5 - j0.866 + 0.5 - j0.866)$$

$$= I_{a1} (-1.732j)$$

The sym. components of phase voltages are

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

On sub $V_c = V_b - I_b Z_f$

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_b - I_b Z_f \end{bmatrix}$$

$$V_{a1} = \frac{1}{3} (V_a + aV_b + a^2V_b - a^2 I_b Z_f)$$

$$3 V_{a1} = V_a + V_b (a + a^2) - a^2 I_b Z_f \rightarrow (5)$$

$$\therefore V_{a2} = \frac{1}{3} (V_a + a^2V_b + aV_b - a I_b Z_f)$$

$$3 V_{a2} = V_a + V_b (a^2 + a) - a I_b Z_f \rightarrow (6)$$

On subtracting eqn 6 from 5

$$\begin{aligned} 3V_{a1} - 3V_{a2} &= V_a + V_b (a + a^2) - a^2 I_b Z_f - V_a \\ &\quad - V_b (a + a^2) + a I_b Z_f \\ &= (-a^2 + a) Z_f I_b \end{aligned}$$


$$\begin{aligned} \text{On } \therefore &= \left(\frac{1}{2} + j \frac{\sqrt{3}}{2} - \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) Z_f I_b \\ &= j \sqrt{3} I_b Z_f \end{aligned}$$

$$\therefore V_{a1} - V_{a2} = j \frac{\sqrt{3}}{3} I_b Z_f = j \frac{1}{\sqrt{3}} I_b Z_f \rightarrow (7)$$

On sub for I_b from eqn 4 in 7

$$\begin{aligned} V_{a1} - V_{a2} &= j \frac{1}{\sqrt{3}} Z_f (-j \sqrt{3} I_{a1}) \\ &= Z_f I_{a1} \rightarrow (8) \end{aligned}$$


The eqns 7 & 8 suggest || el connection of +ve & -ve seq w/ws through a series impedance Z_f .

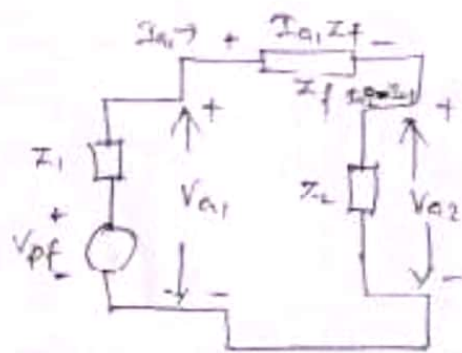

$$I_{a1} = \frac{V_{pf}}{Z_1 + Z_2 + Z_f}$$

$$I_{ff} = I_b = -j\sqrt{3}I_{a1}$$

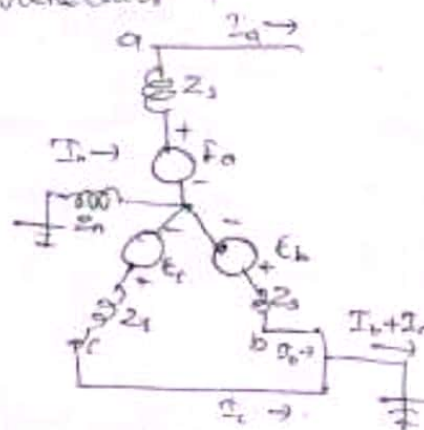Double line to ground fault on an unloaded generator:



fault at $I_f = I_a + I_b + I_c$
Since the generator is unloaded,
the current in phase a is zero.

The conditions at the fault are expressed by the following eqns

$$V_b = 0 ; V_c = 0 ; I_a = 0$$

With $V_b = V_c = 0$, the sym. comp of V s are

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ 0 \\ 0 \end{bmatrix}$$

$$V_{a0} = V_{a1} = V_{a2} = \frac{V_a}{3} \rightarrow 1$$

From the eqn nos of the (1),

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \begin{bmatrix} 0 \\ E_a \\ 0 \end{bmatrix} - \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} \rightarrow 2$$

$$V_{a1} = E_a - Z_1 I_{a1} \rightarrow 2$$

From eqn 1

$$V_{a0} = V_{a1} = V_{a2} \quad \text{Eq from eqn 2}$$

$$V_{a1} = E_a - I_{a1} Z_1$$

On sub these in A

(35)

$$\begin{bmatrix} E_a - I_{a1} Z_1 \\ E_a - I_{a1} Z_1 \\ E_a - I_{a1} Z_1 \end{bmatrix} = \begin{bmatrix} 0 \\ E_a \\ 0 \end{bmatrix} - \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

On rearranging this eqn

$$\begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \begin{bmatrix} 0 \\ E_a \\ 0 \end{bmatrix} - \begin{bmatrix} E_a - I_{a1} Z_1 \\ E_a - I_{a1} Z_1 \\ E_a - I_{a1} Z_1 \end{bmatrix} \rightarrow (B)$$

$$\text{Let } Z = \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix} \therefore Z^{-1} = \begin{bmatrix} 1/Z_0 & 0 & 0 \\ 0 & 1/Z_1 & 0 \\ 0 & 0 & 1/Z_2 \end{bmatrix}$$

To find Z^{-1}

$$Z^{-1} = \frac{\text{Adjoint of } Z}{\text{Determinant of } Z} = \frac{Z_{\text{adj}}}{\Delta Z}$$

$$\Delta Z = \begin{vmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{vmatrix} = Z_0 Z_1 Z_2$$

$$Z_{\text{adj}} = \begin{bmatrix} Z_1 Z_2 & 0 & 0 \\ 0 & Z_0 Z_2 & 0 \\ 0 & 0 & Z_0 Z_1 \end{bmatrix}^T = \begin{bmatrix} Z_1 Z_2 & 0 & 0 \\ 0 & Z_0 Z_2 & 0 \\ 0 & 0 & Z_0 Z_1 \end{bmatrix}$$

$$\therefore Z^{-1} = \frac{1}{Z_0 Z_1 Z_2} \begin{bmatrix} Z_1 Z_2 & 0 & 0 \\ 0 & Z_0 Z_2 & 0 \\ 0 & 0 & Z_0 Z_1 \end{bmatrix} = \begin{bmatrix} 1/Z_0 & 0 & 0 \\ 0 & 1/Z_1 & 0 \\ 0 & 0 & 1/Z_2 \end{bmatrix}$$

On premultiplying the eqn (B) by Z^{-1} we get,

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \begin{bmatrix} 1/Z_0 & 0 & 0 \\ 0 & 1/Z_1 & 0 \\ 0 & 0 & 1/Z_2 \end{bmatrix} \begin{bmatrix} 0 \\ E_a \\ 0 \end{bmatrix} - \begin{bmatrix} 1/Z_0 & 0 & 0 \\ 0 & 1/Z_1 & 0 \\ 0 & 0 & 1/Z_2 \end{bmatrix} \begin{bmatrix} E_a - I_{a1} Z_1 \\ E_a - I_{a1} Z_1 \\ E_a - I_{a1} Z_1 \end{bmatrix}$$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \begin{bmatrix} 0 \\ E_a/Z_1 \\ 0 \end{bmatrix} - \begin{bmatrix} \frac{E_a - I_{a1} Z_1}{Z_0} \\ \frac{E_a - I_{a1} Z_1}{Z_1} \\ \frac{E_a - I_{a1} Z_1}{Z_2} \end{bmatrix}$$

$$\begin{aligned} \text{On multiplying, } I_{a0} &= - \left(\frac{E_a - I_{a1} Z_1}{Z_0} \right) = - \frac{E_a}{Z_0} + \frac{I_{a1} Z_1}{Z_0} \rightarrow \text{I} \\ I_{a1} &= \frac{E_a}{Z_1} - \left(\frac{E_a - I_{a1} Z_1}{Z_1} \right) = \frac{I_{a1} Z_1}{Z_1} = I_{a1} \rightarrow \text{II} \\ I_{a2} &= - \left(\frac{E_a - I_{a1} Z_1}{Z_2} \right) = - \frac{E_a}{Z_2} + \frac{I_{a1} Z_1}{Z_2} \rightarrow \text{III} \end{aligned}$$

(36)

Here $I_a = 0$, On expressing I_a by its symmetrical components we get,

$$I_a = I_{a0} + I_{a1} + I_{a2} = 0 \quad \rightarrow \text{iv}$$

On sub for I_{a0} , I_{a1} & I_{a2} from eqns I, II, III in

$$-\frac{E_a}{Z_0} + \frac{I_{a1} Z_1}{Z_0} + I_{a1} - \frac{E_a}{Z_2} + \frac{I_{a1} Z_1}{Z_2} = 0$$

$$I_{a1} \left(\frac{Z_1}{Z_0} + 1 + \frac{Z_1}{Z_2} \right) = E_a \left(\frac{1}{Z_0} + \frac{1}{Z_2} \right)$$

$$I_{a1} \left(1 + Z_1 \left(\frac{1}{Z_0} + \frac{1}{Z_2} \right) \right) = E_a \left(\frac{1}{Z_0} + \frac{1}{Z_2} \right)$$

$$I_{a1} \left(1 + Z_1 \left(\frac{Z_0 + Z_2}{Z_0 Z_2} \right) \right) = E_a \left(\frac{Z_0 + Z_2}{Z_0 Z_2} \right) \quad \rightarrow \text{v}$$


On multiplying the eqn V throughout by

$$\frac{Z_0 Z_2}{Z_0 + Z_2} \text{ we get}$$

$$I_{a1} \left(\frac{Z_0 Z_2}{Z_0 + Z_2} \right) = E_a$$

$$\therefore I_{a1} = \frac{E_a}{Z_1 + \frac{Z_0 Z_2}{Z_0 + Z_2}} \quad \rightarrow \text{vi}$$

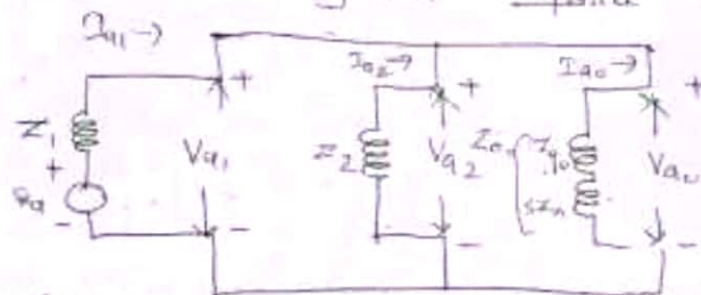Using this eqn, the equivalent circ of (iv) under double line to ground fault can be drawn.



Connection of the seq rlys of an unloaded (v) for a double line to ground fault on phase b & c

Under this fault condition, the seq rlys should be connected in || el since the $+V_0$, $-V_0$ & zero seq voltages are equal during this fault.

In the absence of a ground connection at the (iv) no I can flow into the gnd at the fault. In this case Z_0 would be infinite and I_{a0} would be zero & so the fault will be similar to line to line fault.

Here the fault ct, $I_f = I_b + I_c$
To determine the fault ct, first the sym components I_{a1} , I_{a2} & I_{a0} are calculated using eqns

V, I & III. These eqns are presented here for convenience.

$$I_{a1} = \frac{E_a}{Z_1 + \frac{Z_0 Z_2}{Z_0 + Z_2}}; \quad I_{a0} = -\frac{E_a}{Z_0} + \frac{I_{a1} Z_1}{Z_0}$$

$$I_{a2} = -\frac{E_a}{Z_2} + \frac{I_{a1} Z_1}{Z_2}$$

Alternatively I_{a1} can be calculated using I, then I_{a2} & I_{a0} can be calculated using division rules.

$$I_{a2} = -I_{a1} \times \frac{Z_0}{Z_0 + Z_2}$$

$$I_{a0} = -(I_{a1} - I_{a2})$$

The unbalanced phs I_a, I_b & I_c are related to the sym. components of phs by the following eqn.

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

From this eqn we get


$$I_a = I_{a0} + I_{a1} + I_{a2}$$

$$I_b = I_{a0} + a^2 I_{a1} + a I_{a2}$$

$$I_c = I_{a0} + a I_{a1} + a^2 I_{a2}$$

$$\begin{aligned} \therefore \text{Fault current } I_f &= I_b + I_c \\ &= I_{a0} + a^2 I_{a1} + a I_{a2} + I_{a0} + a I_{a1} + a^2 I_{a2} \\ &= 2 I_{a0} + (a + a^2) I_{a1} + (a + a^2) I_{a2} \\ I_f &= 2 I_{a0} + (a + a^2) (I_{a1} + I_{a2}) \end{aligned}$$

Fault thro an impedance :-

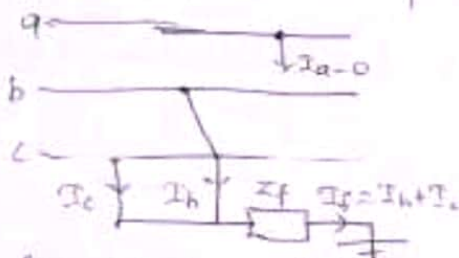

A double line to ground fault at point F in a power sm, thro a fault imp Z_f can be represented by connecting three stubs.

Connection dia of stubs for a double line to gnd fault thro an impedance

The vt & voltage conditions at fault are

$$I_a = 0 \rightarrow 1$$

$$V_b = V_c = Z_f (I_b + I_c) \rightarrow 2$$

The line eqs are gn by

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} \rightarrow 3$$

From row 1 of eqn we get,

$$I_a = I_{a0} + I_{a1} + I_{a2}$$

From eqn 1 we got, $I_a = 0$

$$\therefore I_{a0} + I_{a1} + I_{a2} = 0$$

$$I_{a0} = -(I_{a1} + I_{a2}) \rightarrow 4$$

From row 2, 3

$$I_b = I_{a0} + a^2 I_{a1} + a I_{a2}$$

$$I_c = I_{a0} + a I_{a1} + a^2 I_{a2}$$

$$I_b + I_c = 2I_{a0} + (a^2 + a) I_{a1} + (a + a^2) I_{a2} \rightarrow 5$$

We know that,

$$1 + a + a^2 = 0 \quad \therefore a + a^2 = -1 \rightarrow 6$$

from eqns 5 & 6

$$\begin{aligned} I_b + I_c &= 2I_{a0} - I_{a1} - I_{a2} \\ &= 2I_{a0} - (I_{a1} + I_{a2}) \rightarrow 7 \end{aligned}$$

From eqn 4

$$I_b + I_c = 2I_{a0} - (-I_{a0}) = 3I_{a0} \rightarrow 8$$

The sym. components of voltages after substituting

$V_c = V_b$ are gn by

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

from row 1,

$$V_{a0} = \frac{1}{3} (V_a + V_b + V_c) = \frac{1}{3} (V_a + 2V_b) \rightarrow (9)$$

from row 2 & 3

$$\begin{aligned} V_{a1} &= V_{a2} = \frac{1}{3} (V_a + aV_b + a^2V_b) \\ &= \frac{1}{3} (V_a + (a + a^2)V_b) \\ &= \frac{1}{3} (V_a - V_b) \quad (\because a + a^2 = -1) \end{aligned} \rightarrow (10)$$

from eqn 9 & 10 we can write,

$$\begin{aligned} V_{a0} - V_{a1} &= \frac{1}{3} (V_a + 2V_b) - \frac{1}{3} (V_a - V_b) \\ &= \frac{1}{3} (V_a + 2V_b - V_a + V_b) = V_b \rightarrow (11) \end{aligned}$$

On substituting for V_b from eqn 2 in 11


$$V_{a0} - V_{a1} = Z_f (I_b + I_c)$$

On substituting $(I_b + I_c)$ from eqn 8

$$V_{a0} - V_{a1} = Z_f 3 I_{a0}$$

$$V_{a0} - V_{a1} + 3 Z_f I_{a0} \rightarrow 12$$
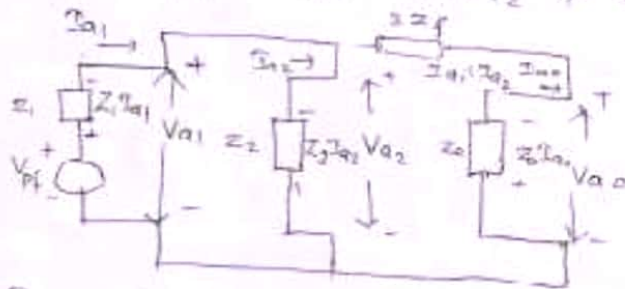
$$\text{Also } V_{a0} = V_{a2} + 3 Z_f I_{a0} \rightarrow 13$$



From fig $I_{a1} = \frac{V_{pf}}{Z_1 + \frac{Z_2(Z_0 + 3Z_f)}{Z_2 + Z_0 + 3Z_f}} \rightarrow 14$

$$V_{a1} = V_{pf} - Z_1 I_{a1} \rightarrow 15$$

$$V_{a2} = V_{a1} ; I_{a2} = \frac{V_{a2}}{Z_2} ; I_{a0} = -(I_{a1} + I_{a2}) \rightarrow 16$$

From fig (1) eqn 8

$$\text{Fault current } I_f = I_b + I_c = 3 I_{a0}$$